

Design #4

Zine-Eddine Haboussi

March 18, 2025

1 Problem statement and Specifications

Design a single-ended amplifier using common-source configuration with a diode-connected load to meet the following specifications:

Specification	Value
DC Gain	6 dB
Bandwidth	≥ 10 GHz
Power Consumption	≤ 1.5 mW
Capacitive Load	50 fF

2 Analysis

$$I_D \leq \frac{P_{cons}}{V_{DD}} \leq \frac{1.5 \cdot 10^{-3}}{1.8} \leq 0.83 \text{ mA}$$

$$GBW = \frac{g_{m1}}{2\pi C_{out}} \geq 2 \cdot 10 \cdot 10^9 \implies g_{m1} \geq 6.28 \text{ mS}$$

We assume $g_{m1} = 15 \text{ mS}$, thus $(\frac{g_m}{I_D})_1 = 18.07$

$$A_v = g_{m1} R_{out} \Rightarrow R_{out} = \frac{2}{15 \text{ m}} = 133.33 \Omega$$

We assume $r_{o1} \gg \frac{1}{g_{m2}}$

$$\frac{1}{g_{m2}} = 150 \Rightarrow g_{m2} = 6.7 \text{ mS} \Rightarrow (\frac{g_m}{I_D})_2 = 8$$





$$r_{o1} = \frac{R_{out} \cdot (\frac{1}{g_{m2}})}{(\frac{1}{g_{m2}}) - R_{out}} = 1200 \Omega$$

$$\frac{g_m}{g_{ds}} = g_{m1}r_{o1} = 18$$

From charts:


- $g_m/g_{ds} = 17.67$ (intrinsic gain).
- $V_{GS} = 0.63V$
- $W_1 = 138 \mu m, L_1 = 150nm$.
- $W_2 = 216 \mu m, L_2 = 350nm$.

3 gm/ID Charts

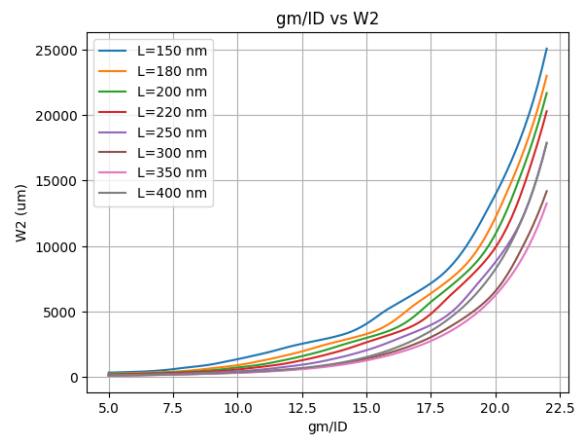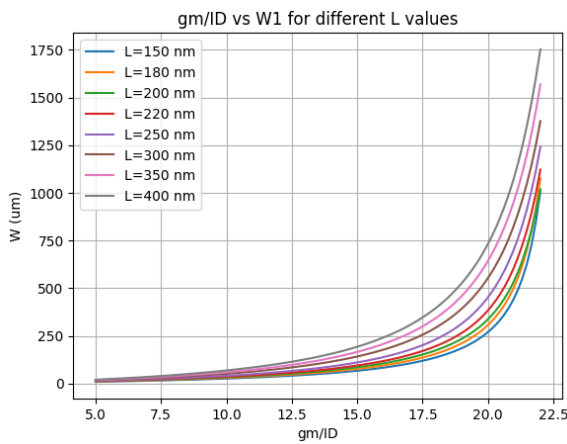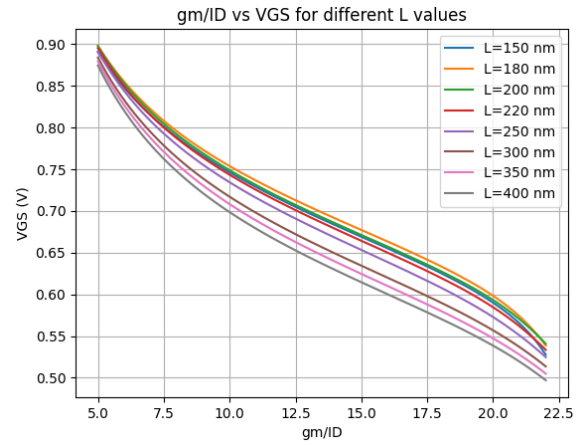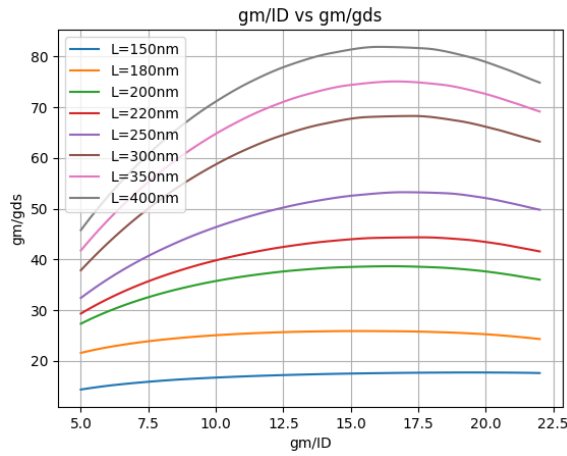

4 Simulation Results

4.1 Test bench

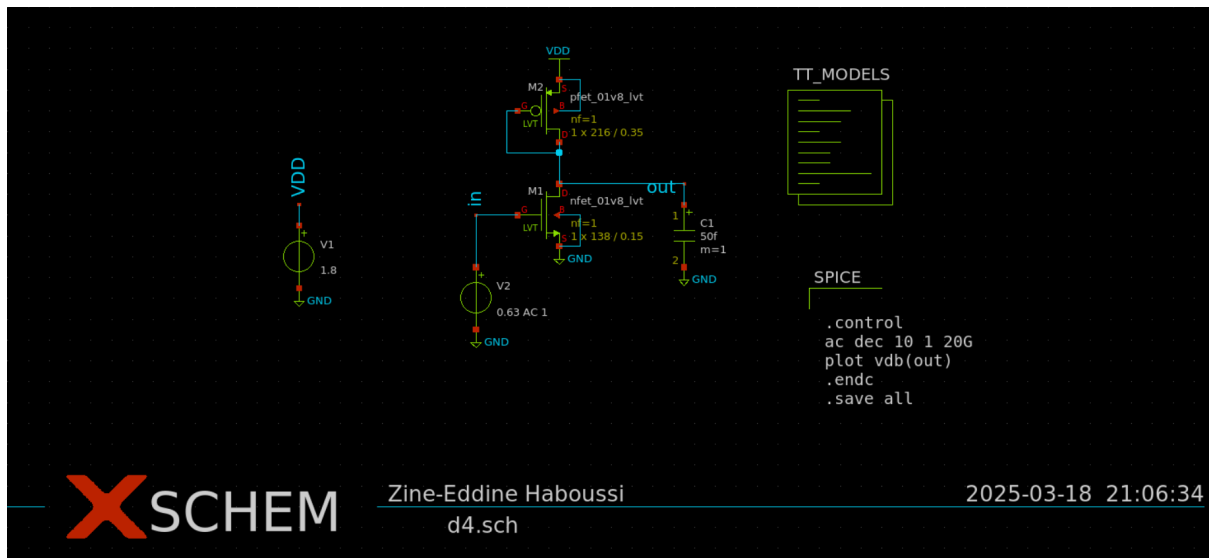

4.2 AC Analysis

